

Instructor: Zhenyu (Henry) Huang
(509) 372-6781, zhenyu.huang@pnl.gov

EE 521: Analysis of Power Systems

Lecture 3 *Power Flow*

Fall 2009

Mondays & Wednesdays 5:45-7:00

August 24 – December 18

Test 216

Topics

- Power Flow Basics
 - Bus Types
 - Nodal Admittance Matrix
 - Equation Derivation
- Solution Methods
 - Newton-Raphson
 - Decouple Power Flow
 - DC Power Flow


Power Flow

- One of the basic tools for examining a power system
- Used in planning studies
- Based on the concept of node injections
- A non-linear problem that generally requires an iterative solution

Power Flow Basics


- The problem: solve electrical circuits, but at a large scale

Bus Type	Boundary Conditions				Unknowns				Total Number of Buses of the Type
	P	Q	V	θ	P	Q	V	θ	
PV									r
PQ									$N-r-1$
V θ									1

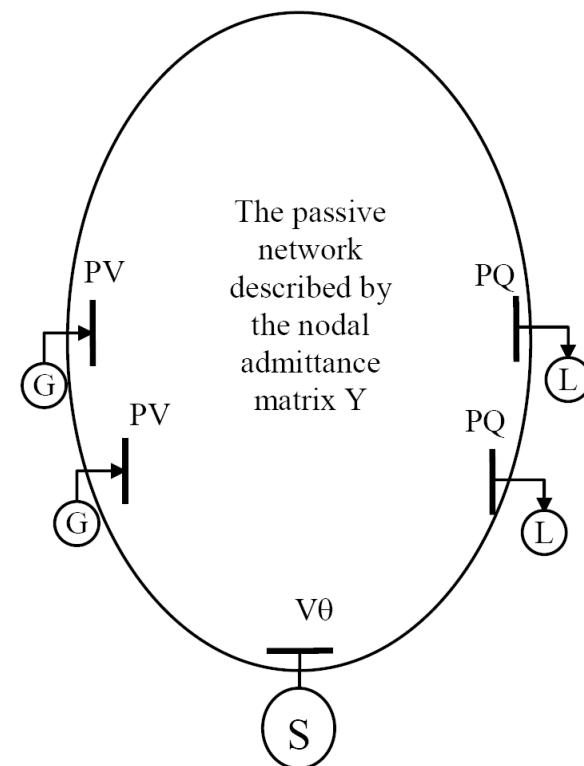

A Simple Circuit


Linear Problem

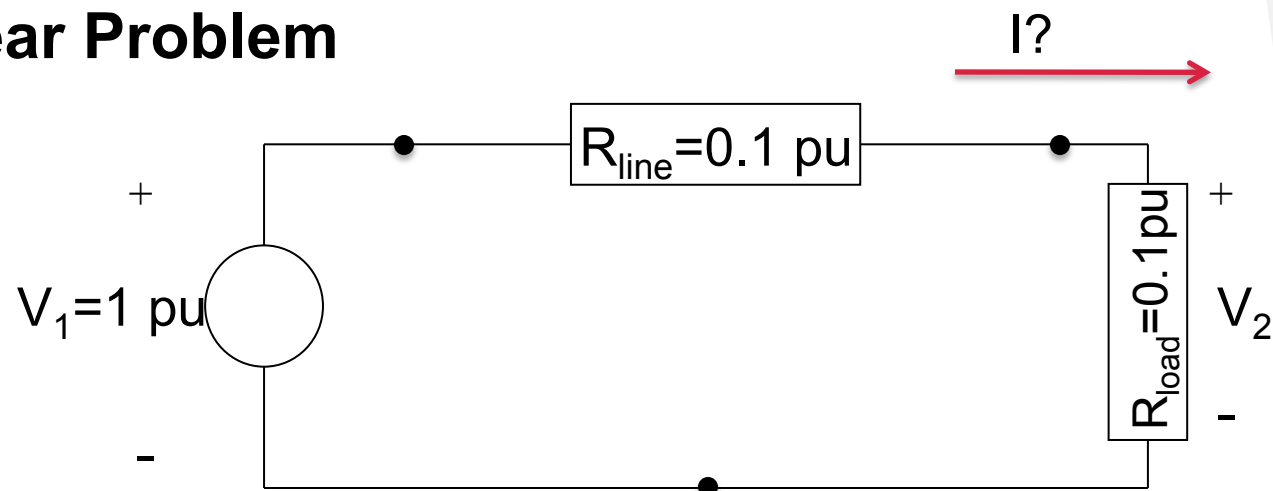

$$I = YV = \frac{1}{0.1 + 0.1} = 5 \text{ pu}$$

Still a Simple Circuit

Non-linear Problem

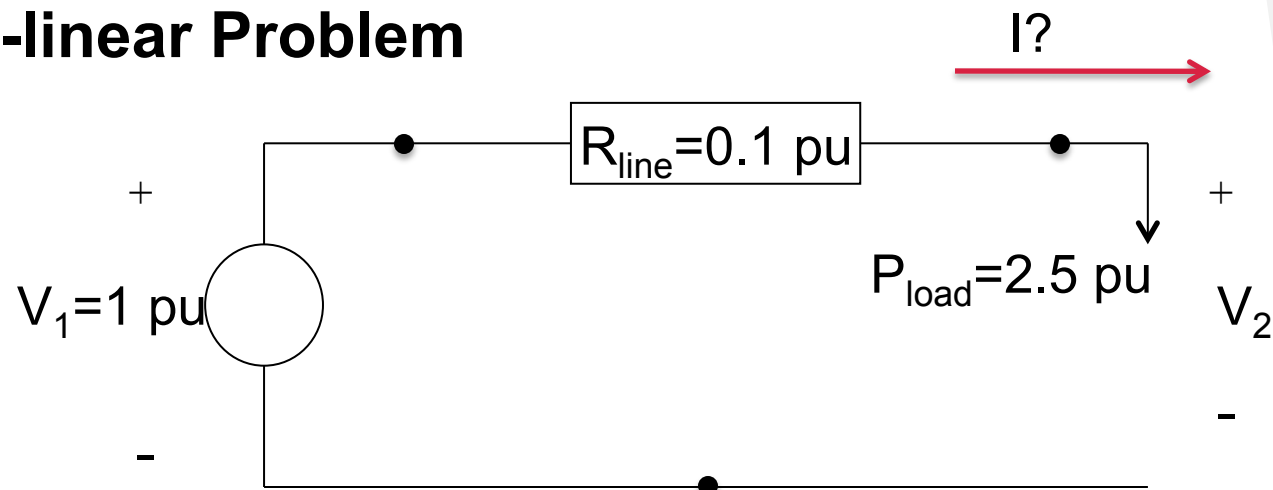

~~$$I = YV = \frac{1}{0.1 + 0.1} = 5 \text{ pu}$$~~

$$\begin{cases} I = \frac{V_1 - V_2}{R_{\text{line}}} \\ P_{\text{load}} = V_2 I \end{cases} \quad P_{\text{load}} = V_2 I = V_2 \frac{V_1 - V_2}{R_{\text{line}}} \quad V_2^2 - V_1 V_2 + P_{\text{load}} R_{\text{line}} = 0$$

$$V_2^2 - V_2 + 0.25 = 0 \quad V_2 = 0.5 \text{ or } -0.5 \text{ pu} \quad I = 5 \text{ pu}$$


A Simple Power System

$$I = YV$$

$$Y = \begin{bmatrix} y_{12} + y_{13} & -y_{12} & -y_{13} \\ -y_{12} & y_{12} + y_{23} & -y_{23} \\ -y_{13} & -y_{23} & y_{13} + y_{23} \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$
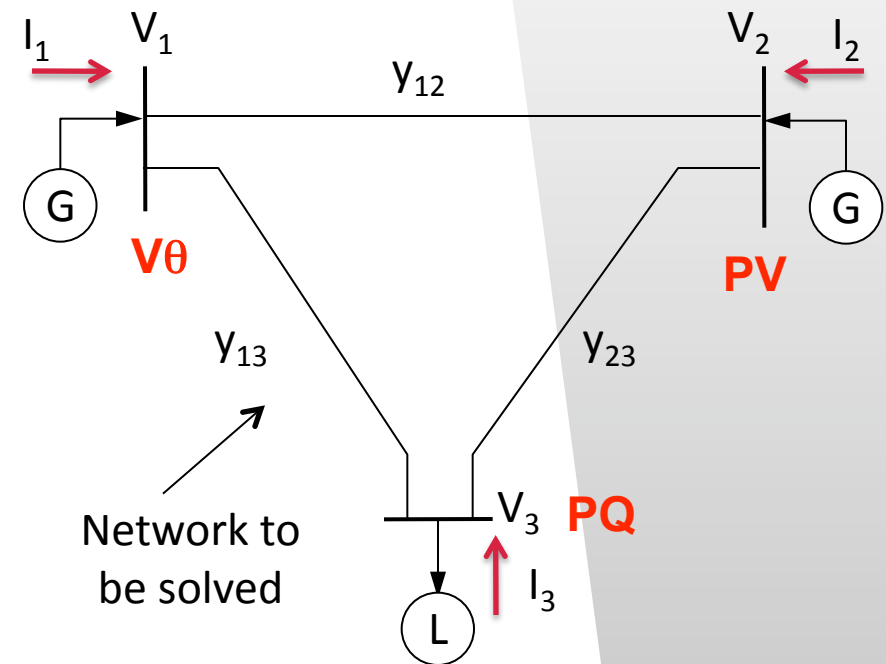
$$\begin{bmatrix} V_1^* & 0 & 0 \\ 0 & V_2^* & 0 \\ 0 & 0 & V_3^* \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1^* & 0 & 0 \\ 0 & V_2^* & 0 \\ 0 & 0 & V_3^* \end{bmatrix} \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$




A Simple Power System

$$E^* I = E^* Y V$$

$$\begin{cases} P_1 - jQ_1 = |V_1|^2 Y_{11} + V_1^* V_2 Y_{12} + V_1^* V_3 Y_{13} \\ P_2 - jQ_2 = |V_2|^2 Y_{22} + V_2^* V_1 Y_{21} + V_2^* V_3 Y_{23} \\ P_3 - jQ_3 = |V_3|^2 Y_{33} + V_3^* V_1 Y_{31} + V_3^* V_2 Y_{32} \end{cases} \quad \underline{Y = G + jB}$$

$$\begin{cases} P_1 = |V_1|^2 G_{11} + |V_1||V_2|(G_{12} \cos(\theta_2 - \theta_1) - B_{12} \sin(\theta_2 - \theta_1)) \\ \quad + |V_1||V_3|(G_{13} \cos(\theta_3 - \theta_1) - B_{13} \sin(\theta_3 - \theta_1)) \\ Q_1 = -|V_1|^2 B_{11} - |V_1||V_2|(G_{12} \sin(\theta_2 - \theta_1) + B_{12} \cos(\theta_2 - \theta_1)) \\ \quad - |V_1||V_3|(G_{13} \sin(\theta_3 - \theta_1) + B_{13} \cos(\theta_3 - \theta_1)) \end{cases}$$


$$\begin{cases} P_1 = |V_1| \sum_{j=1}^N |V_j| (G_{1j} \cos(\theta_j - \theta_1) - B_{1j} \sin(\theta_j - \theta_1)) \\ Q_1 = -|V_1| \sum_{j=1}^N |V_j| (G_{1j} \sin(\theta_j - \theta_1) + B_{1j} \cos(\theta_j - \theta_1)) \end{cases}$$

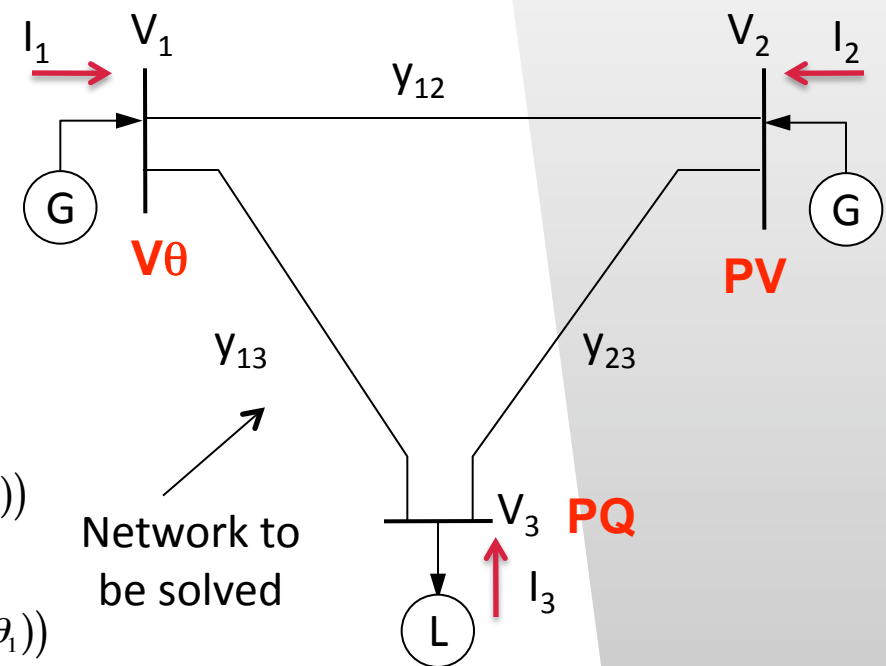

A Simple Power System

$$\begin{array}{l}
 \text{V}\theta \left\{ \begin{array}{l} V_1 = \text{known} \\ \theta_1 = \text{known} \end{array} \right. \\
 \text{PV} \left\{ \begin{array}{l} P_2 = f_{P2}(|V_1|, |V_2|, |V_3|, \theta_1, \theta_2, \theta_3) \\ V_2 = \text{known} \end{array} \right. \\
 \text{PQ} \left\{ \begin{array}{l} P_3 = f_{P3}(|V_1|, |V_2|, |V_3|, \theta_1, \theta_2, \theta_3) \\ Q_3 = f_{Q3}(|V_1|, |V_2|, |V_3|, \theta_1, \theta_2, \theta_3) \end{array} \right.
 \end{array}$$

$$\begin{cases}
 P_2 = |V_2| \sum_{j=1}^N |V_j| (G_{2j} \cos(\theta_j - \theta_2) - B_{2j} \sin(\theta_j - \theta_2)) \\
 P_3 = |V_3| \sum_{j=1}^N |V_j| (G_{3j} \cos(\theta_j - \theta_3) - B_{3j} \sin(\theta_j - \theta_3)) \\
 Q_3 = -|V_3| \sum_{j=1}^N |V_j| (G_{3j} \sin(\theta_j - \theta_3) + B_{3j} \cos(\theta_j - \theta_3))
 \end{cases}$$

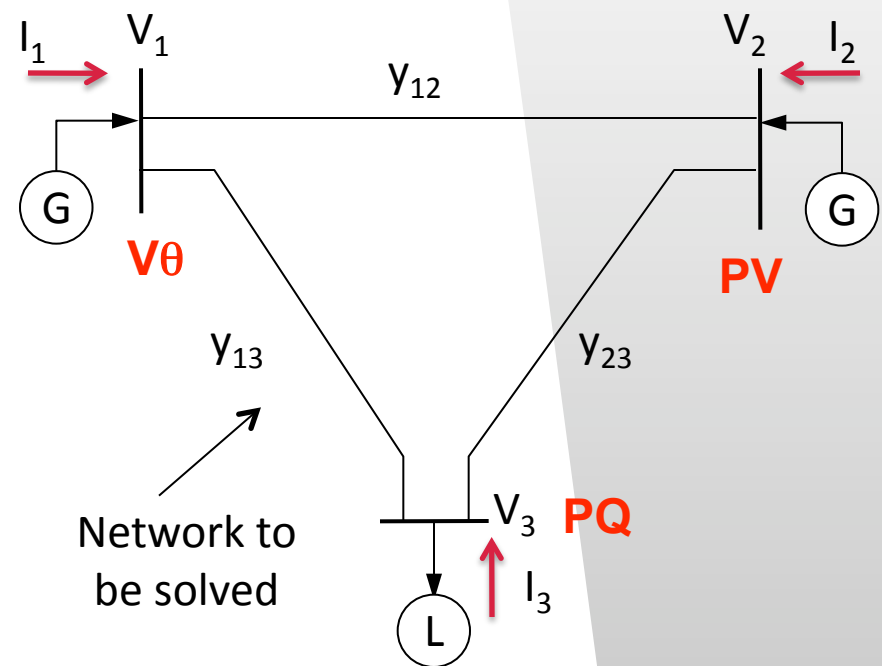


A Simple Power System

$$Y = \begin{bmatrix} -j14 & j10 & j4 \\ j10 & -j12 & j2 \\ j4 & j2 & -j6 \end{bmatrix}$$

$$\begin{cases} P_2 = |V_2| \sum_{j=1}^N |V_j| (G_{2j} \cos(\theta_j - \theta_2) - B_{2j} \sin(\theta_j - \theta_2)) \\ P_3 = |V_3| \sum_{j=1}^N |V_j| (G_{3j} \cos(\theta_j - \theta_3) - B_{3j} \sin(\theta_j - \theta_3)) \\ Q_3 = -|V_3| \sum_{j=1}^N |V_j| (G_{3j} \sin(\theta_j - \theta_3) + B_{3j} \cos(\theta_j - \theta_3)) \end{cases}$$

$$\begin{cases} P_2 = 1.5 = 1.05 \cdot [-1 \cdot 10 \cdot \sin(-\theta_2) - |V_3| \cdot 2 \cdot \sin(\theta_3 - \theta_2)] \\ P_3 = -1 = |V_3| \cdot [-1 \cdot 4 \cdot \sin(-\theta_3) - 1.05 \cdot 2 \cdot \sin(\theta_2 - \theta_3)] \\ Q_3 = -0.25 = -|V_3| \cdot [1 \cdot 4 \cdot \cos(-\theta_3) + 1.05 \cdot 2 \cdot \cos(\theta_2 - \theta_3) - |V_3| \cdot 6] \end{cases}$$

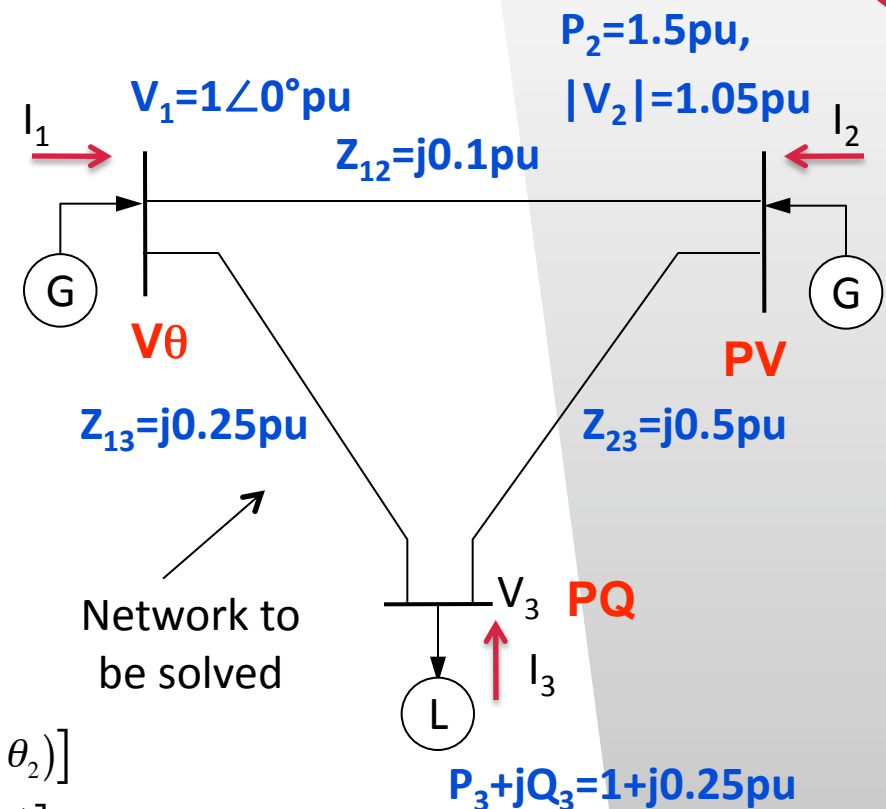

Power Flow Solution Methods


- Gauss-Seidel
- Newton-Raphson
- Decoupled
- DC

Newton-Raphson Method

- The basic principle
 - Guess the solution
 - Try and evaluate how far away from the true solution
 - If too far away, adjust your guess and try again
- The key is how to adjust the guess
 - Slope (Derivative)

$$f(x) = 0$$
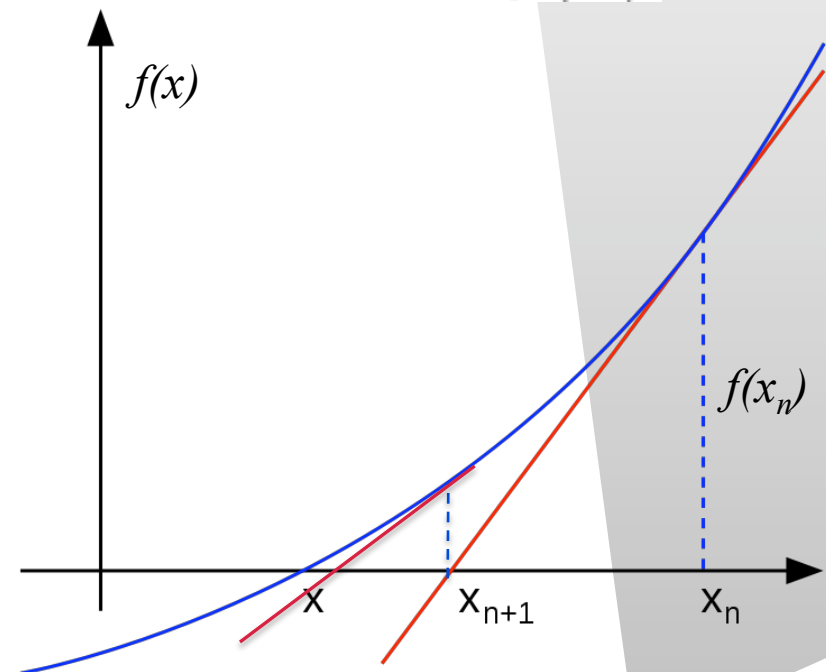
$$x_{n+1} = x_n - \frac{f(x_n)}{f'(x_n)}$$



Newton-Raphson Method for Power Flow Solution

- Jacobian Matrix
- Newton-Raphson Power Flow Procedure
 - First guess
 - “flat start” or a known point
 - The first guess is important
 - Evaluate power equations $f(x)$
 - Evaluate Jacobian matrix $J(x)$
 - Adjust guess point x

$$x^{n+1} = x^n - J(x^n)^{-1} f(x^n)$$

$$f(x) = P_i(x) - P_i = 0$$

$$J(x) = \begin{bmatrix} \frac{\partial P}{\partial \theta} & \frac{\partial P}{\partial V} \\ \frac{\partial Q}{\partial \theta} & \frac{\partial Q}{\partial V} \end{bmatrix}$$


$$[J(x)] \begin{bmatrix} \Delta \theta \\ \Delta V \end{bmatrix} = \begin{bmatrix} \Delta P(x) \\ \Delta Q(x) \end{bmatrix}$$

$$\begin{bmatrix} \theta^{n+1} \\ V^{n+1} \end{bmatrix} = \begin{bmatrix} \theta^n \\ V^n \end{bmatrix} - [J(x^n)]^{-1} \begin{bmatrix} \Delta P(x^n) \\ \Delta Q(x^n) \end{bmatrix}$$

Newton-Raphson Power Flow Example

$$\begin{cases} P_2 = 1.5 \\ \quad = 1.05 \cdot [1 \cdot 10 \cdot \sin(-\theta_2) - |V_3| \cdot 2 \cdot \sin(\theta_3 - \theta_2)] \\ P_3 = 1 \\ \quad = |V_3| \cdot [1 \cdot 4 \cdot \sin(-\theta_3) - 1.05 \cdot 2 \cdot \sin(\theta_2 - \theta_3)] \\ Q_3 = 0.25 \\ \quad = -|V_3| \cdot [1 \cdot 4 \cdot \cos(-\theta_3) + 1.05 \cdot 2 \cdot \cos(\theta_2 - \theta_3) - |V_3| \cdot 6] \end{cases}$$

$$\begin{bmatrix} \theta^{n+1}_2 \\ \theta^{n+1}_3 \\ V^{n+1}_3 \end{bmatrix} = \begin{bmatrix} \theta^n_2 \\ \theta^n_3 \\ V^n_3 \end{bmatrix} - \begin{bmatrix} \frac{\partial P_2}{\partial \theta_2} & \frac{\partial P_2}{\partial \theta_3} & \frac{\partial P_2}{\partial V_3} \\ \frac{\partial P_3}{\partial \theta_2} & \frac{\partial P_3}{\partial \theta_3} & \frac{\partial P_3}{\partial V_3} \\ \frac{\partial Q_3}{\partial \theta_2} & \frac{\partial Q_3}{\partial \theta_3} & \frac{\partial Q_3}{\partial V_3} \end{bmatrix}^{-1} \begin{bmatrix} P_2(x_n) - 1.5 \\ P_3(x_n) - 1 \\ Q_3(x_n) - 0.25 \end{bmatrix}$$

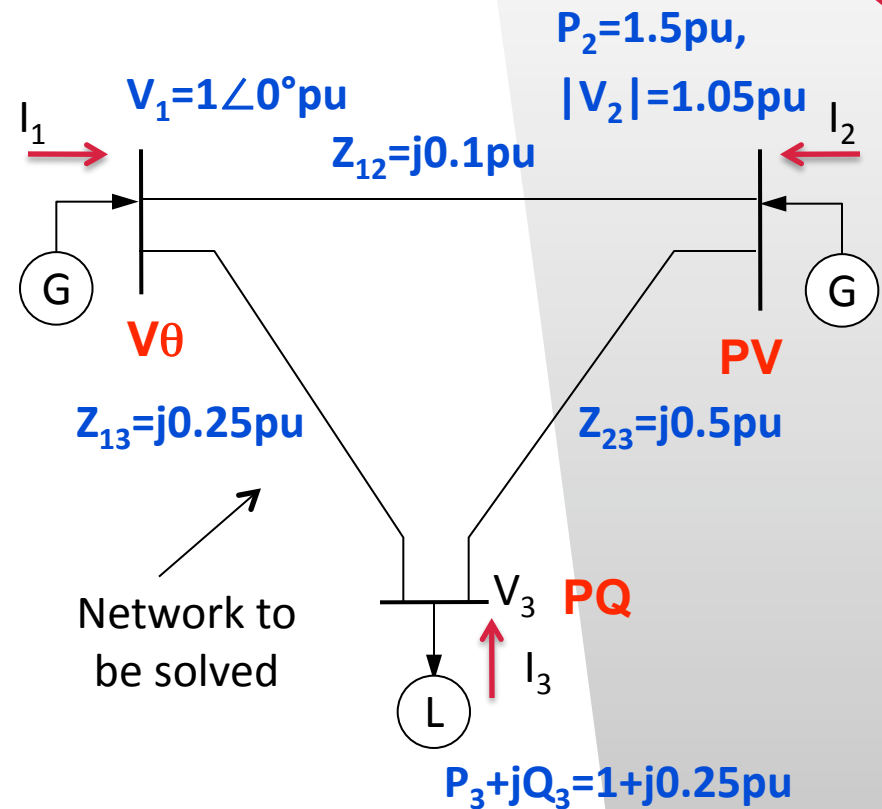

Newton-Raphson Power Flow Example

t



	Initial	1	2	3	4
Theta 2	0	5.546556	5.593182	5.593524	5.593524
Theta 3	0	-7.43451	-7.88595	-7.89849	-7.89849
Voltage 3	1	0.9745	0.95735	0.956977	0.956977

Decoupled Power Flow

- The objective
 - Reduce computation in evaluating Jacobian matrix
- The basic principle
 - $\Delta\theta$ primarily affects P
 - ΔV primarily affects Q

$$J(x) = \begin{bmatrix} \frac{\partial P}{\partial \theta} & \frac{\partial P}{\partial V} \\ \frac{\partial Q}{\partial \theta} & \frac{\partial Q}{\partial V} \end{bmatrix} \approx \begin{bmatrix} \frac{\partial P}{\partial \theta} & 0 \\ 0 & \frac{\partial Q}{\partial V} \end{bmatrix}$$

$$\begin{bmatrix} \theta^{n+1} \\ V^{n+1} \end{bmatrix} = \begin{bmatrix} \theta^n \\ V^n \end{bmatrix} - [J(x^n)]^{-1} \begin{bmatrix} \Delta P(x^n) \\ \Delta Q(x^n) \end{bmatrix}$$




$$\begin{cases} \theta^{n+1} = \theta^n - \left[\frac{\partial P}{\partial \theta} \right]^{-1} [\Delta P(\theta^n)] \\ V^{n+1} = V^n - \left[\frac{\partial Q}{\partial V} \right]^{-1} [\Delta Q(V^n)] \end{cases}$$

Re-examination of Power Flow Equations

$$E^* I = E^* Y V$$

$$\begin{cases} P_i = |V_i| \sum_{j=1}^N |V_j| (G_{ij} \cos(\theta_j - \theta_i) - B_{ij} \sin(\theta_j - \theta_i)) \\ Q_i = -|V_i| \sum_{j=1}^N |V_j| (G_{ij} \sin(\theta_j - \theta_i) + B_{ij} \cos(\theta_j - \theta_i)) \end{cases}$$

$$\begin{cases} \frac{\partial P_i}{\partial \theta_j} = -|V_i| |V_j| (G_{ij} \sin(\theta_j - \theta_i) + B_{ij} \cos(\theta_j - \theta_i)) \\ |V_j| \frac{\partial Q_i}{\partial |V_j|} = -|V_i| |V_j| (G_{ij} \sin(\theta_j - \theta_i) + B_{ij} \cos(\theta_j - \theta_i)) \\ \frac{\partial P_i}{\partial \theta_i} = |V_i| \sum_{\substack{j=1 \\ j \neq i}}^N |V_j| (G_{ij} \sin(\theta_j - \theta_i) + B_{ij} \cos(\theta_j - \theta_i)) = -Q_i - |V_i|^2 B_{ii} \\ |V_i| \frac{\partial Q_i}{\partial |V_i|} = -|V_i| \sum_{\substack{j=1 \\ j \neq i}}^N |V_j| (G_{ij} \sin(\theta_j - \theta_i) + B_{ij} \cos(\theta_j - \theta_i)) - 2|V_i|^2 B_{ii} = Q_i - |V_i|^2 B_{ii} \end{cases}$$

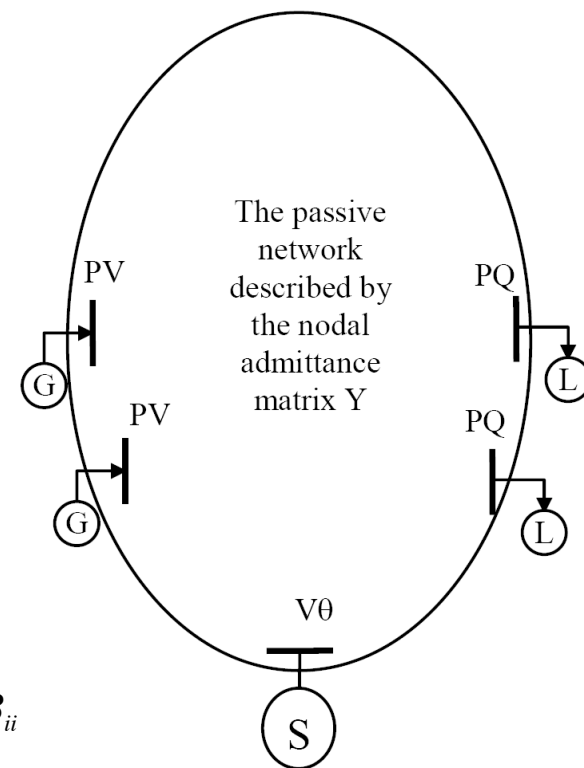

Re-examination of Power Flow Equations

$$\left\{ \begin{array}{l} \frac{\partial P_i}{\partial \theta_j} = -|V_i||V_j|(G_{ij} \sin(\theta_j - \theta_i) + B_{ij} \cos(\theta_j - \theta_i)) \\ |V_j| \frac{\partial Q_i}{\partial |V_j|} = -|V_i||V_j|(G_{ij} \sin(\theta_j - \theta_i) + B_{ij} \cos(\theta_j - \theta_i)) \\ \frac{\partial P_i}{\partial \theta_i} = |V_i| \sum_{\substack{j=1 \\ j \neq i}}^N |V_j| (G_{ij} \sin(\theta_j - \theta_i) + B_{ij} \cos(\theta_j - \theta_i)) = -Q_i - |V_i|^2 B_{ii} \\ |V_i| \frac{\partial Q_i}{\partial |V_i|} = -|V_i| \sum_{\substack{j=1 \\ j \neq i}}^N |V_j| (G_{ij} \sin(\theta_j - \theta_i) + B_{ij} \cos(\theta_j - \theta_i)) - 2|V_i|^2 B_{ii} = Q_i - |V_i|^2 B_{ii} \end{array} \right.$$



$$\left\{ \begin{array}{l} \frac{\partial P_i}{\partial \theta_j} = -|V_i||V_j| B_{ij} \\ |V_j| \frac{\partial Q_i}{\partial |V_j|} = -|V_i||V_j| B_{ij} \\ \frac{\partial P_i}{\partial \theta_i} = -|V_i|^2 B_{ii} \\ |V_i| \frac{\partial Q_i}{\partial |V_i|} = -|V_i|^2 B_{ii} \end{array} \right.$$



$$\left. \begin{array}{l} \cos(\theta_j - \theta_i) \approx 1 \\ \sin(\theta_j - \theta_i) \approx \theta_j - \theta_i \\ B_{ij} \gg G_{ij} \end{array} \right\} \Rightarrow G_{ij} \sin(\theta_j - \theta_i) \ll B_{ij} \cos(\theta_j - \theta_i)$$

$$Q_i \ll |V_i|^2 B_{ii}$$

Further Decoupled Power Flow

$$\begin{cases} [\theta^{n+1}] = [\theta^n] - \left[\frac{\partial P}{\partial \theta} \right]^{-1} [\Delta P(\theta^n)] \\ [V^{n+1}] = [V^n] - \left[\frac{\partial Q}{\partial V} \right]^{-1} [\Delta Q(V^n)] \end{cases}$$



$$\begin{cases} [\theta^{n+1}] = [\theta^n] - [-B]^{-1} \left[\frac{\Delta P(\theta^n)}{|V|} \right] \\ [V^{n+1}] = [V^n] - [-B]^{-1} \left[\frac{\Delta Q(V^n)}{|V|} \right] \end{cases}$$

Decoupled Power Flow Procedure

- Make a guess
- Calculate $\Delta P/V$
- Update θ
- Use new θ to calculate $\Delta Q/V$
- Update V
- Repeat until ΔP & ΔQ within tolerance
- **Assignment (due: Sept 9):**
 - 1. Derive the decoupled power flow equations
 - 2. Solve the 3-bus example using the decoupled power flow procedure

$$\begin{cases} [\theta^{n+1}] = [\theta^n] - [-B]^{-1} \left[\frac{\Delta P(\theta^n)}{|V|} \right] \\ [V^{n+1}] = [V^n] - [-B]^{-1} \left[\frac{\Delta Q(V^n)}{|V|} \right] \end{cases}$$

DC Power Flow

- Assumptions
 - All transfer conductance values are set to zero i.e. $G_{ij}=0$
 - Small angle assumption
 - All voltages are set to 1 pu
- Properties
 - Not an accurate power flow solution – only calculate real power flow
 - Becomes a linear problem
 - Used for quick system assessment

$$\cos(\theta_j - \theta_i) \approx 1$$

$$\sin(\theta_j - \theta_i) \approx \theta_j - \theta_i$$

$$\begin{cases} P_i = |V_i| \sum_{j=1}^N |V_j| (G_{ij} \cos(\theta_j - \theta_i) - B_{ij} \sin(\theta_j - \theta_i)) \\ Q_i = -|V_i| \sum_{j=1}^N |V_j| (G_{ij} \sin(\theta_j - \theta_i) + B_{ij} \cos(\theta_j - \theta_i)) \end{cases}$$

$$[-B][\theta] = [P]$$

WASHINGTON STATE UNIVERSITY



TRI-CITIES

World Class. Face to Face.

Questions?



Gauss-Seidel

- First effective method to be implemented on digital computers
- In general has a linear convergence rate
- Can generally accept a “flat start”
- Has some issues with reactance reactance branches
- Each bus is treated individually

Newton-Raphson

- Based on the concept of driving an error function to zero
- Generally has a quadratic convergence rate
- Some issues exist with “flat start” values
- Each iteration requires more computations than for a Gauss-Seidel, but quadratic convergence results in fewer iterations
- Very robust, but the values of the Jacobian must be updated at each iteration

Decoupled Power Flow

- Exploits the decoupled nature of voltage and angle, thus reducing the number of non-zero entries in the Jacobian
- Assumptions are made that greatly improve the convergence time
- When the assumptions are not true, convergence issues may arise

DC Power Flow

- Linear/non-iterative solution to the power flow problem
- Will only calculate the MW flows in the system, not MVAR
- Effective for situations requiring an approximate solution, e.g. contingency analysis